

Roll No.

D-3823

B. C. A. (Part I) EXAMINATION, 2020

(Old Course)

Paper Third

INTRODUCTORY ELECTRONICS

(101)

Time : Three Hours]

[Maximum Marks : 50

Note : Attempt any *two* parts from each question. All questions carry equal marks.

Unit—I

1. (a) What is semiconductor ? Write down the various features of semiconductor.
- (b) What is transistor ? Describe the working of CE amplifier.
- (c) What do you understand by Logic Family ? Distinguish among various IC logic families.

Unit—II

2. (a) What is IC ? Discuss merits and demerits of IC.

(A-33) P. T. O.

[2]

- (b) Write down the steps to construct resistor and capacitor in a monolithic integrated circuit.
- (c) Write short notes on the following :
 - (i) P-Substrate
 - (ii) Epitaxial n layer

Unit—III

- 3. (a) Perform the following :
 - (i) $(10110)_2 - (101)_2$ by 2's complement
 - (ii) $(FA7C)_{16} = (?)_8$
- (b) What is 8421 code ? Write down the advantages and disadvantages of this code.
- (c) What do you understand by Gray Code ? Write down the steps to convert gray code to binary code.

Unit—IV

- 4. (a) Which are Universal Gates ? Why are they called Universal Gates ?
- (b) Prove that :
$$\overline{(A+B)} = \bar{A} - \bar{B}$$
- (c) What do you mean by SOP and POS Boolean form ? Explain it with suitable examples.

Unit—V

- 5. (a) Draw and explain Half adder combinational circuit.
- (b) Draw and explain JK-flip-flop with suitable diagram.
- (c) What is Multiplexer ? Draw and explain 4×1 MUX ?